




# A Whirlwind Tour of PIN Diodes

Nick Cardamone – Fall 2023 – Nonlinear Microwave Devices  
(and Circuit Theory 1 Tutorial)

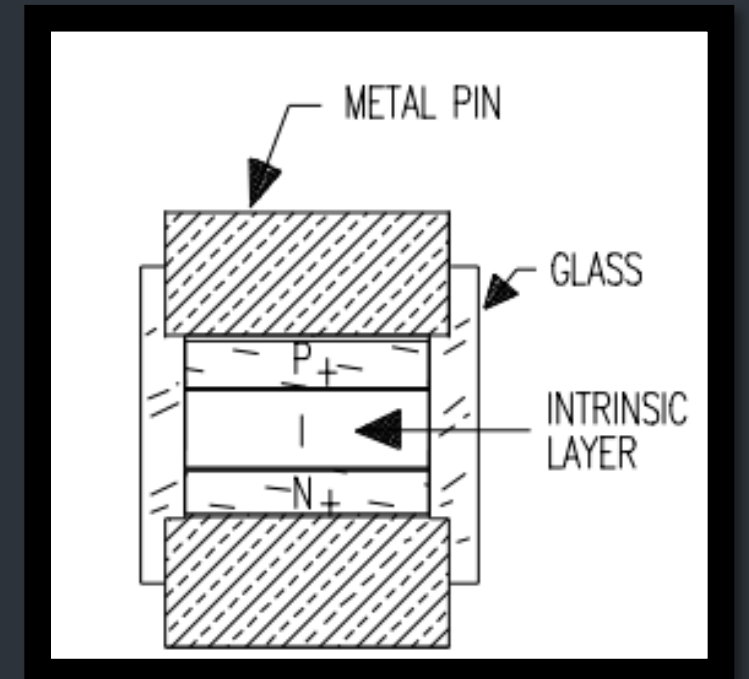
# Overview – Applications of PIN Diodes

- ▶ What is a diode?
- ▶ Diode Models – DC/ Low Frequency, High Frequency
- ▶ PIN Diode Overview + Model
- ▶ PIN Diode Switches
- ▶ PIN Diode Attenuators
- ▶ PIN Diode Modulators
- ▶ PIN Diode Phase Shifters
- ▶ PIN Diode Detectors





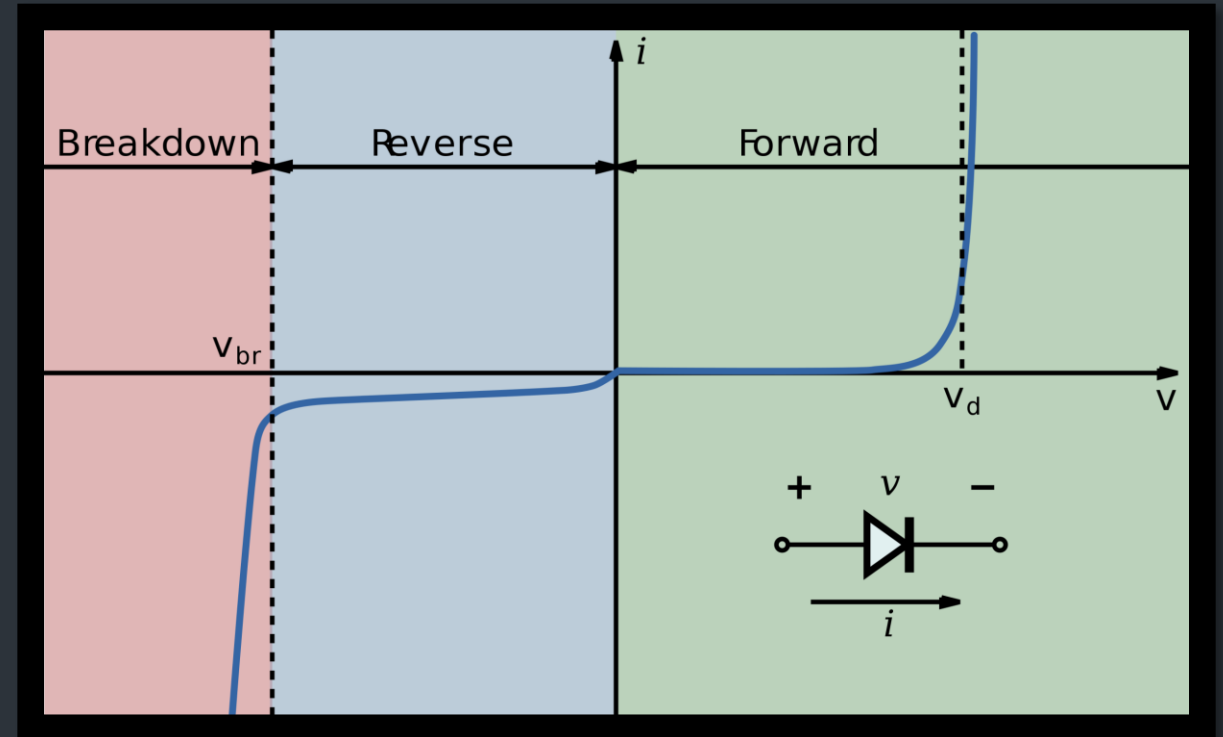
# What is a Diode?

- ▶ 2 Terminal Non-Linear Device
- ▶ Only allows DC current to flow in 1 direction
- ▶ Symbol looks similar to an arrow
- ▶ The current is supposed to flow in the direction of the arrow



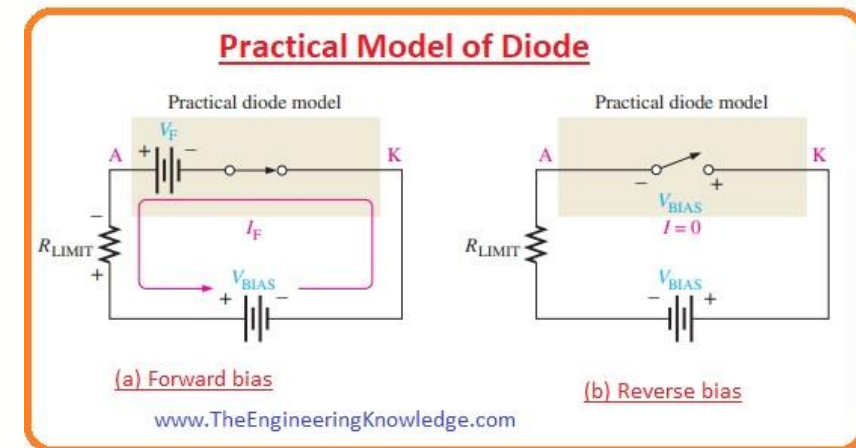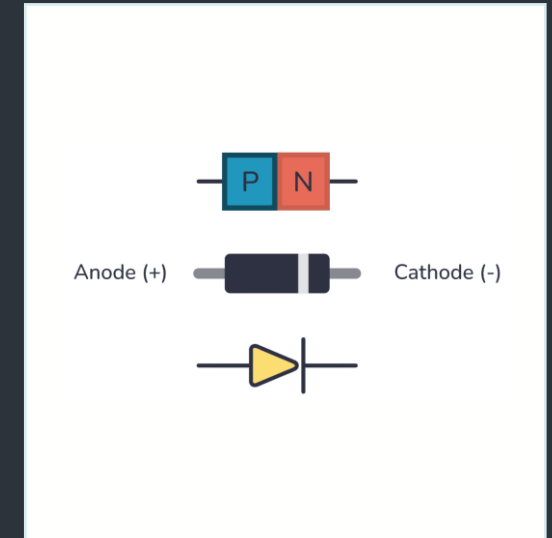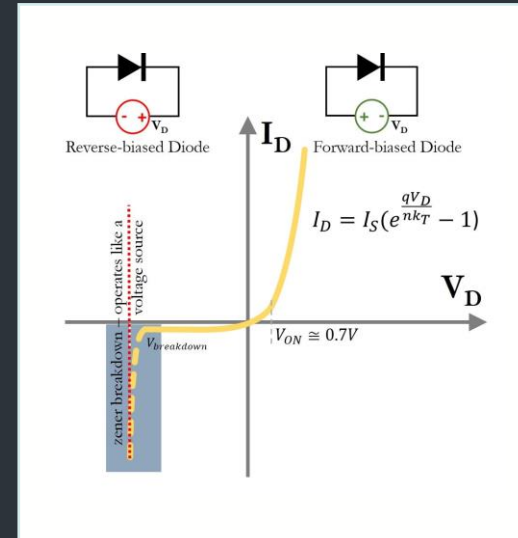
# Diode Modeling (Low Frequency/ DC)

- ▶ A Diode acts like a voltage controlled switch
- ▶ If the DC voltage supplied to the diode is sufficiently positive the diode acts as a short circuit (forward bias)
- ▶ If the DC voltage supplied to the diode is negative the diode acts like an open circuit (reverse bias)
- ▶ The DV voltage supplied to the diode is called the bias voltage
- ▶ In forward bias, the DC voltage across the diode will be constant regardless of the current



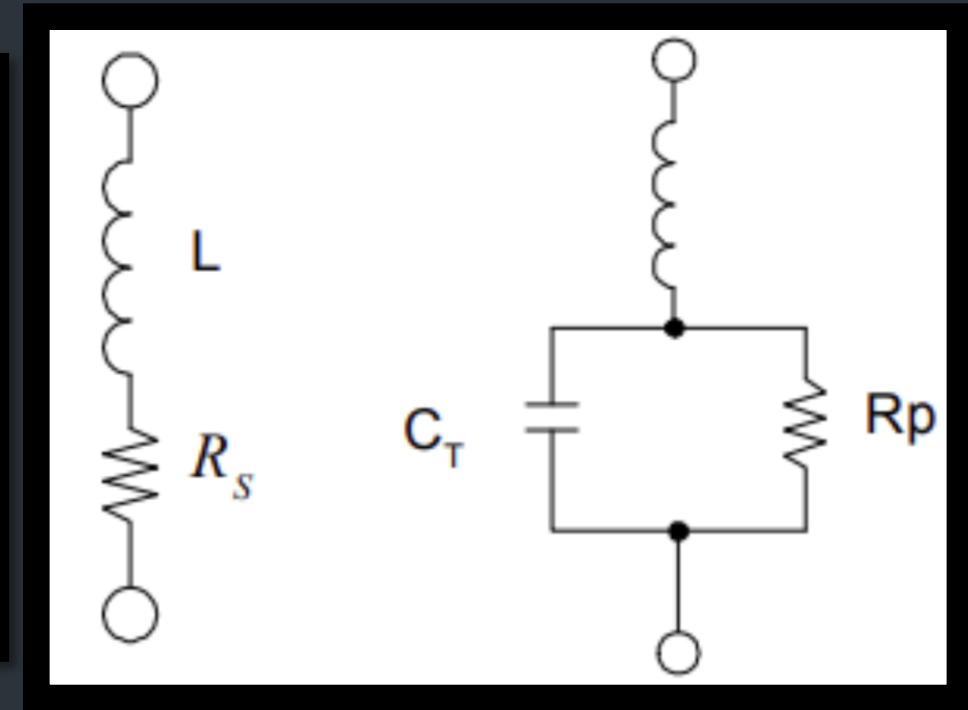
# Diode Modeling (High Frequency)

- ▶ When the diode is forward biased, it acts like a series inductor and resistor
- ▶ When the diode is in reverse bias, it acts like a parallel resistor and capacitor (similar to a varactor)


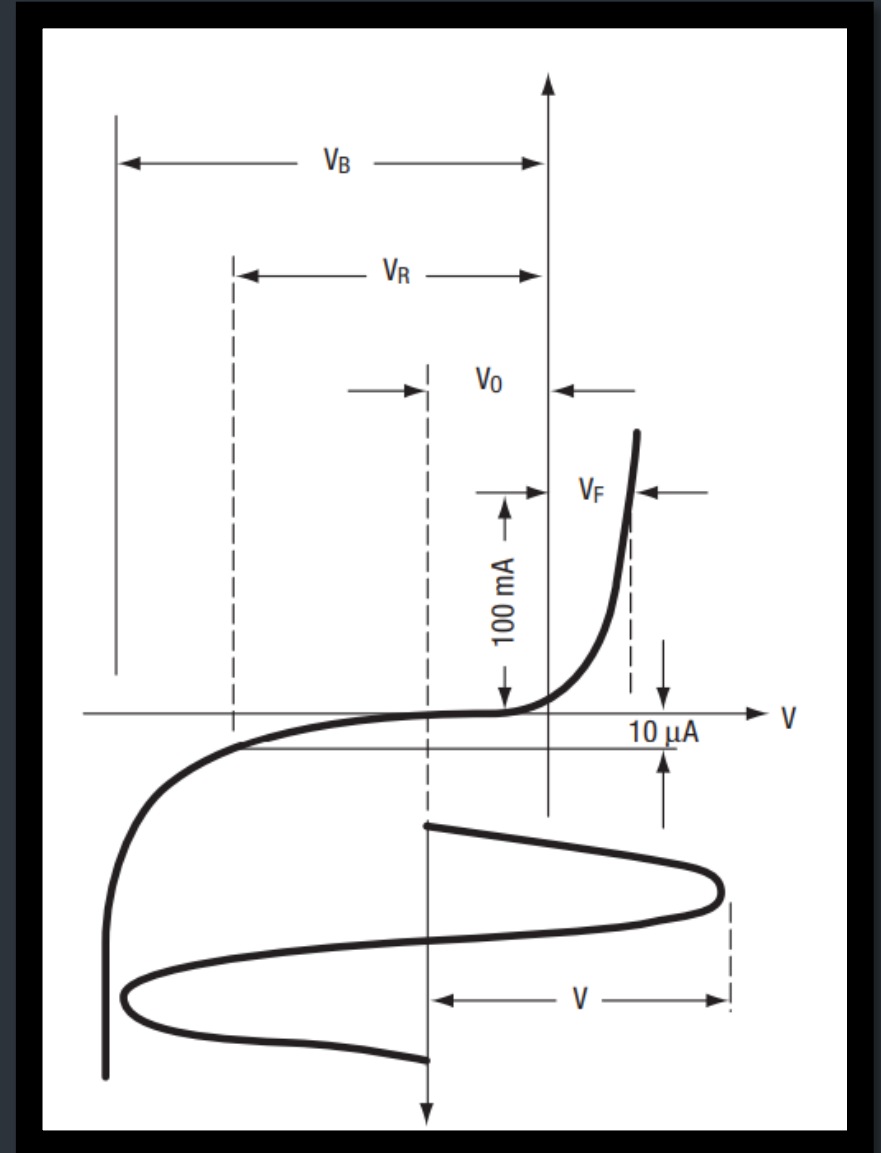
# PIN Diodes

- ▶ An Intrinsic layer is inserted in between the P and N regions of a typical diode
- ▶ That intrinsic layer is lightly doped or not doped at all
- ▶ This allows the junction to store extra charge which increases the reverse recovery time of the diode significantly
- ▶ This means that the diode can conduct in both directions provided the stored charge is not depleted
  - ▶ i.e. either the frequency needs to be high enough or there need to be enough bias current





# PIN Diode Forward Bias

The PIN diode acts as a current controlled resistor in forward bias  
Also acts like a voltage controlled capacitor in reverse bias

$$R_s = \frac{W^2}{(\mu_n + \mu_p)Q} = \frac{W^2}{(\mu_n + \mu_p)\tau I_{fwd}}, \text{ for } f > \frac{1300}{W^2}$$

Where:

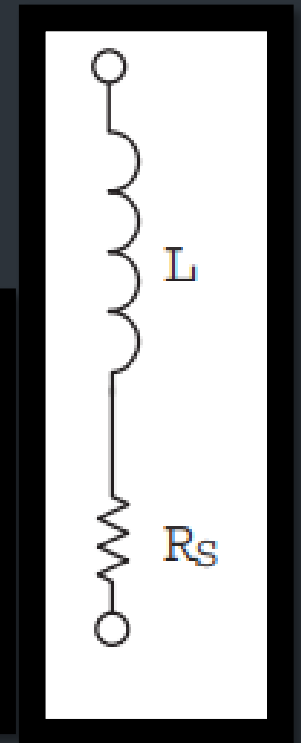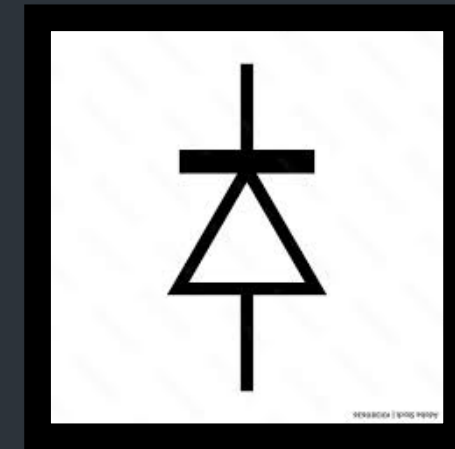- $R_s$  is the series resistance of the PIN diode ( $\Omega$ )
- $W$  is the width of the intrinsic region ( $\mu\text{m}$ )
- $f$  is the frequency of operation (MHz)
- $\tau$  is the carrier lifetime
- $\mu_n$  is the electron mobility
- $\mu_p$  is the hole mobility








# PIN Diode Applications

- ▶ RF (High Frequency) Switches – great for switching large RF powers with small bias currents
- ▶ Variable Attenuators (variable voltage dividers – controlled by bias current)
- ▶ Modulators
- ▶ Phase Shifters
- ▶ Optical Detectors (used in fiber communication systems)



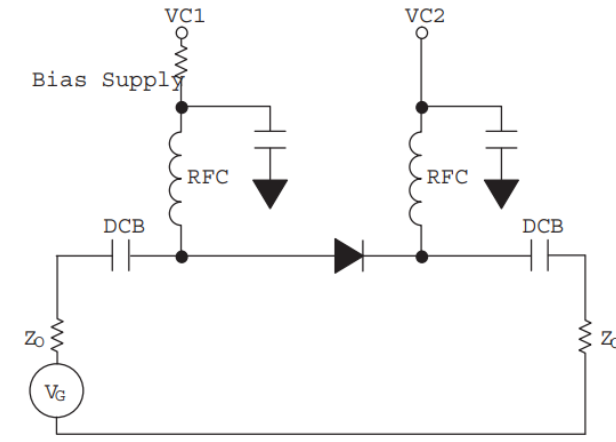
# PIN Diode Switches

- ▶ Diodes can either be used in series or in parallel (shunt)
- ▶ These type of switches either transmit the signal or reflect it back
- ▶ Isolation is a problem with series switches




A. Series SPST Switch

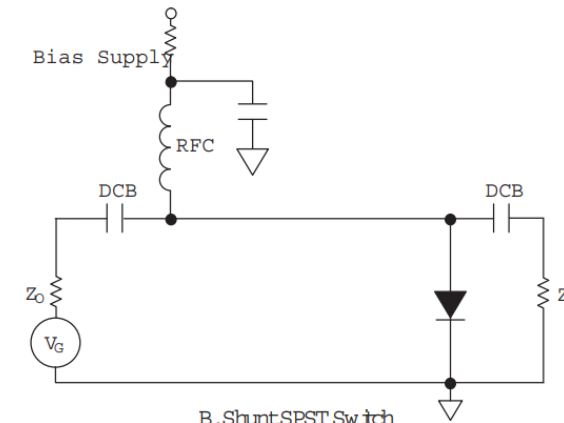

B. Shunt SPST Switch

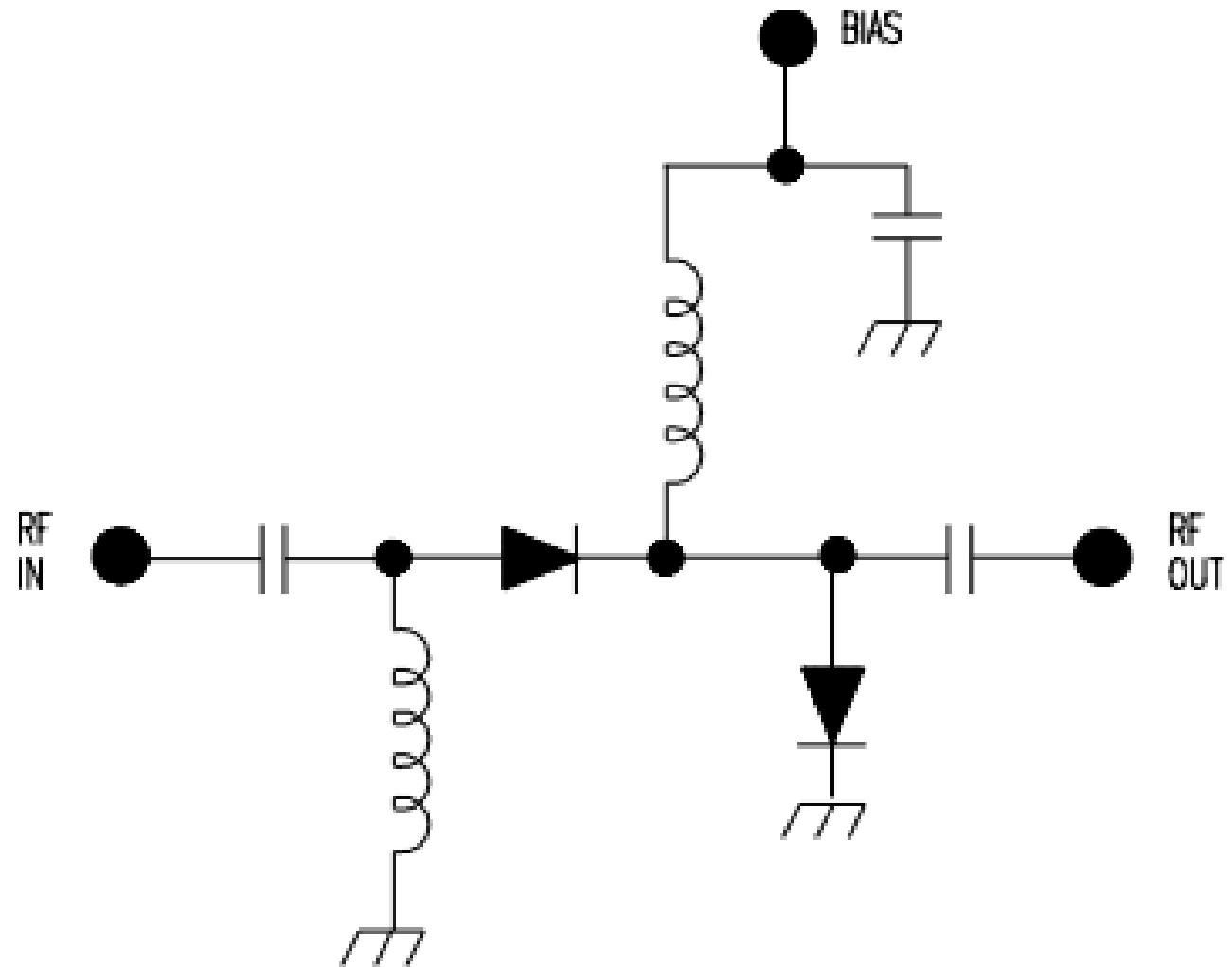
# Compound Switches

- ▶ Multiple diodes can be used to improve the isolation




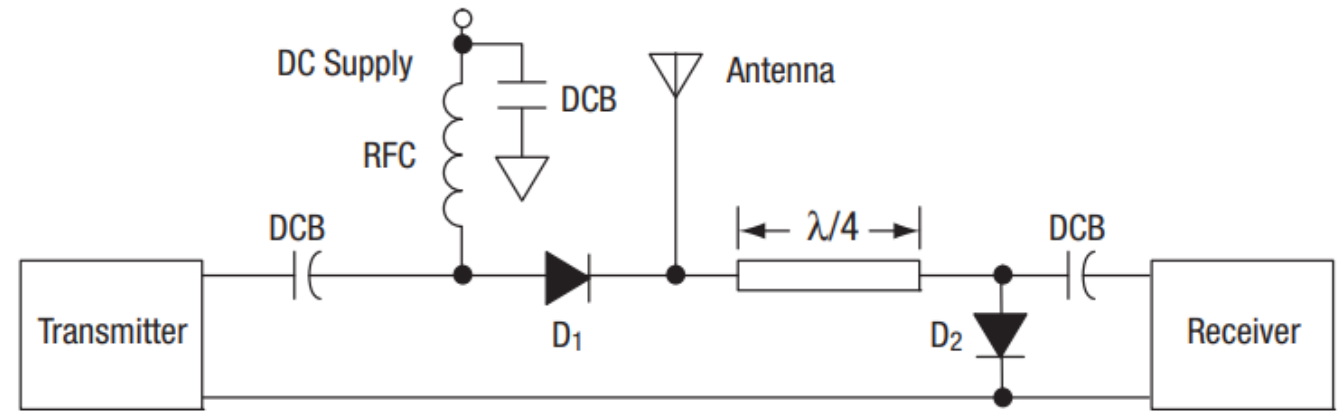
# PIN Diode TX/ RX Switch Example

- ▶ Single pole double throw
- ▶ Quarter wave transformer is used to do impedance transformation



A. Antenna Switch Using  $\lambda/4$  Line Length

# High Frequency Switch Example

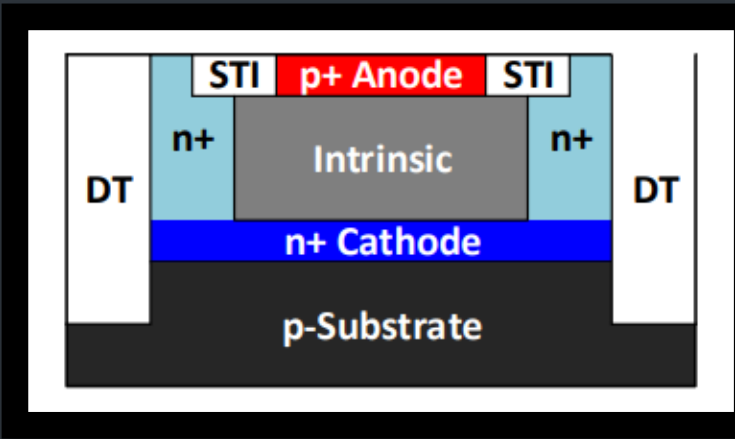
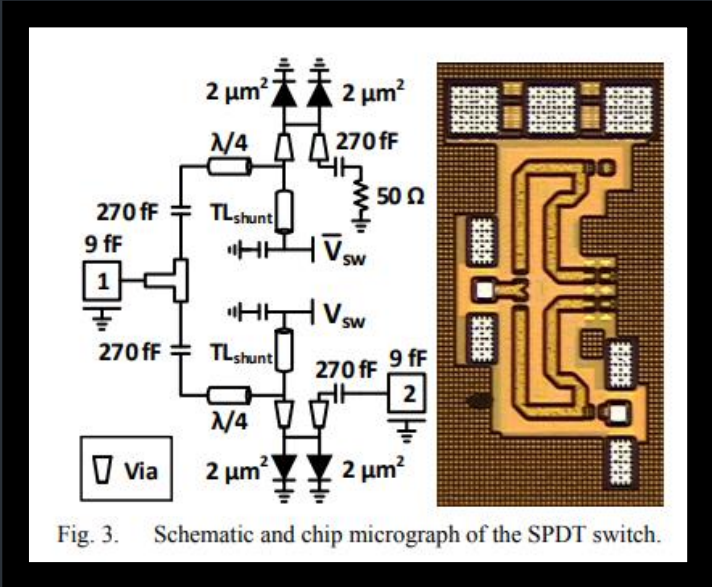




Reference	[5]	[6]	[7]	[8]	This Work
Technology	GaAs	130nm SiGe	130nm SiGe	90nm SiGe	<b>90nm SiGe</b>
Device	PIN	nMOS	PIN	HBT	<b>PIN</b>
Topology	$\lambda/4$ shunt	$\lambda/4$ shunt	Series-shunt	$\lambda/4$ shunt	<b><math>\lambda/4</math> shunt</b>
Freq. (GHz)	75-110	85-105	50-78	77-110	<b>73-133</b>
Insertion Loss (dB)	1.1-1.6	2.3-3.0	2.0-2.7	1.4-2.0	<b>1.4-2.0*</b>
Isolation (dB)	21-22	20-21	25-35	17.5-19	<b>19-22</b>
$P_{1dB}$ (dBm)	-	-	-	+19	<b>&gt; +24**</b>
Area (mm <sup>2</sup> )	0.94	0.05	0.11	0.14	<b>0.14</b>

\* Aluminum pads have not been de-embedded.  
 \*\* Limited by available source power.
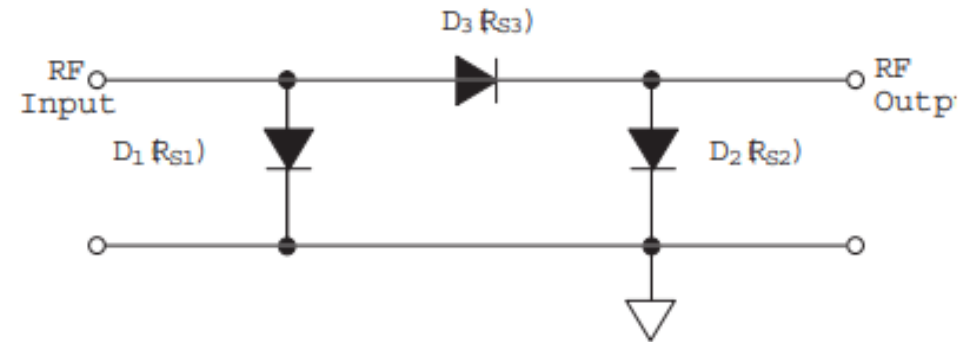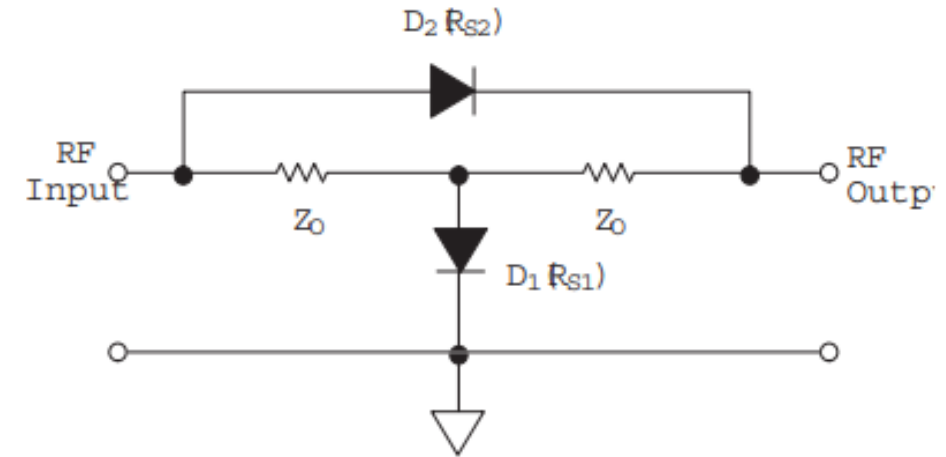
# Matched PIN Diode Attenuators

- ▶ An attenuator is just a voltage divider
- ▶ Which is meant to add some loss in the circuit to make the voltages smaller at the output
- ▶ Any PIN diode switch can be used as an attenuator, all that is needed is to control the bias current more finely
- ▶ In the matched attenuator, each diode is biased at a different current level
- ▶ The bias of each diode must track one another at all attenuation levels to maintain matching
- ▶ The bias circuit is not shown



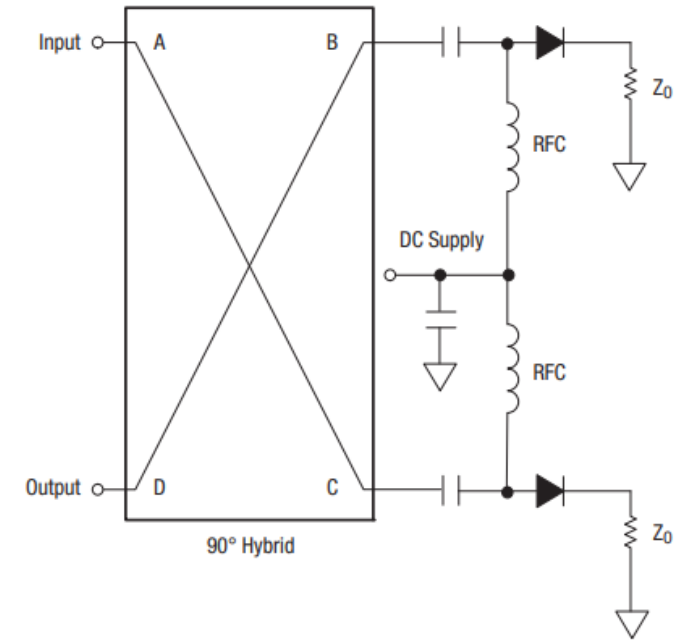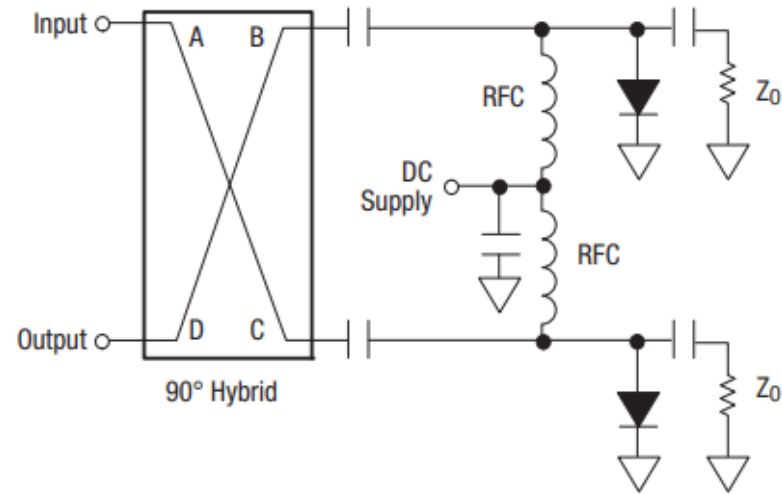



# Tuned PIN Diode Attenuators

The matching is from the 90 degree hybrid (coupler)



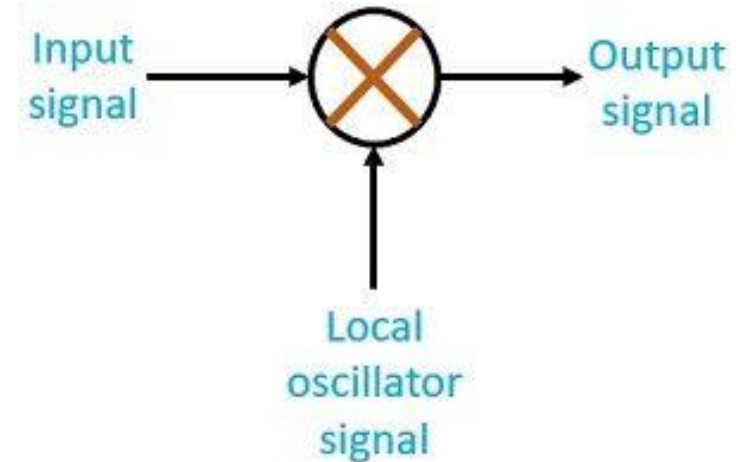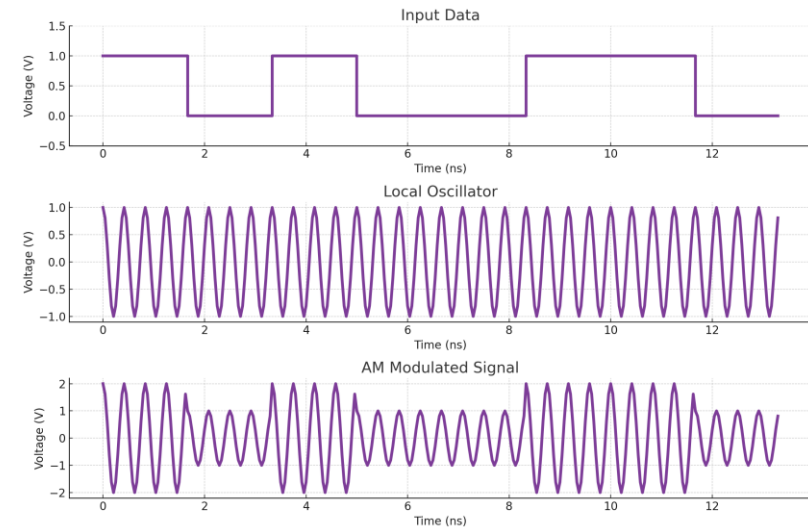
# Modulators and Modulation

- ▶ To modulate a signal, just use a multiplication block (called a mixer)
- ▶ We modulate signals because it is easier to transmit higher frequency signals with antennas
- ▶  $v_{out}(t) = (bias + data(t)) * V_0 \cos(2\pi f_0 t)$



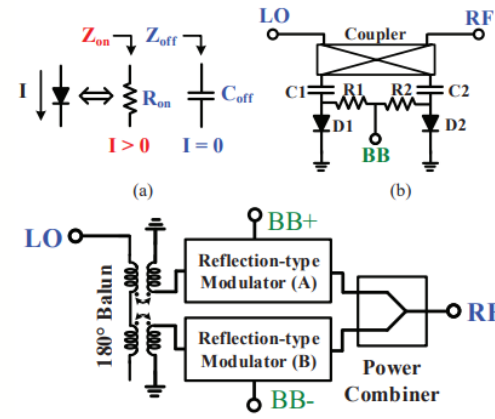
# PIN Diode Modulators

- Since the  $R_s$  of a PIN diode is a function of the bias current, this can be used for modulation
- Modulation Bandwidth can be limited due to the (relatively long reverse recovery time)



Double Balanced Mixer

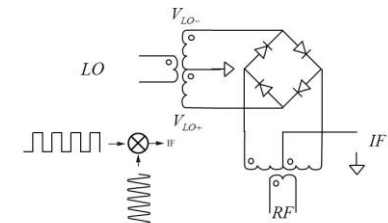

$$V_{RF}(t) \cdot V_{LO}(t) = A_{RF} \sin(\omega_{RF}t) \times \sin(\omega_{LO}t)$$

$$= \frac{2}{\pi} A_{RF} \left[ \cos(\omega_{RF} - \omega_{LO})t + \frac{1}{3} \cos(3(\omega_{RF} - \omega_{LO})t) + \dots \right]$$



© D.S. Ricketts 2012-2015 www.rickettslab.org/radiosystemdesign

19


Reference	MMIC Process	Frequency (GHz)	LO Driving Power (dBm)	Modulation BW (MHz)	Phase Im. (°)	Amplitude Im. (dB)	EVM @ symbol rate 1 MS/s (%)	Chip Size (mm <sup>2</sup> )
[5]	1-μm HBT	50 - 110	-8	3	5	2.5	<6	1×1
[6]	0.13-μm CMOS	25 - 55	12	15			4	0.64×0.67
[7]	2-μm GaAs	30 - 50	0	3000			<11	1×1
[8]	0.13-μm CMOS	15 - 75	4	>1000	3	0.5	3	0.5×0.35
[9]	0.5-μm GaAs HEMT	30 - 130	-10	>1000	5	0.8	<5	0.8×0.7
[10]	0.1-μm InP HEMT	115 - 135		10000	5	0.2	5	1×2
<b>This work</b>	<b>GaAs PIN Diode</b>	<b>25 - 65</b>	<b>-15</b>	<b>&gt;500</b>	<b>&lt;6</b>	<b>&lt;0.9</b>	<b>&lt;4</b>	<b>0.7×0.8</b>
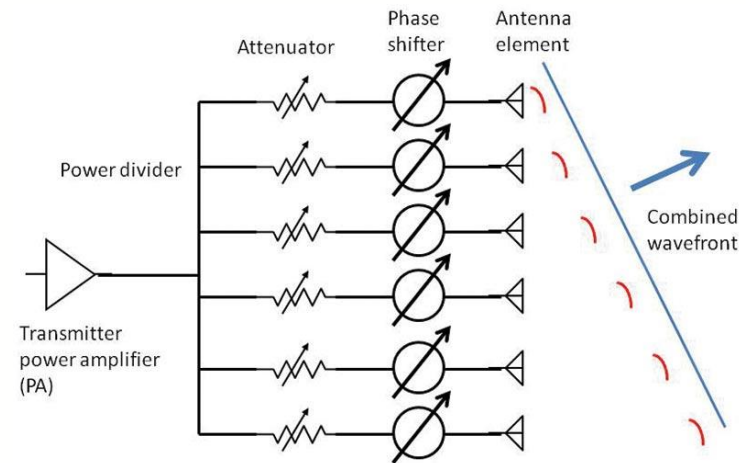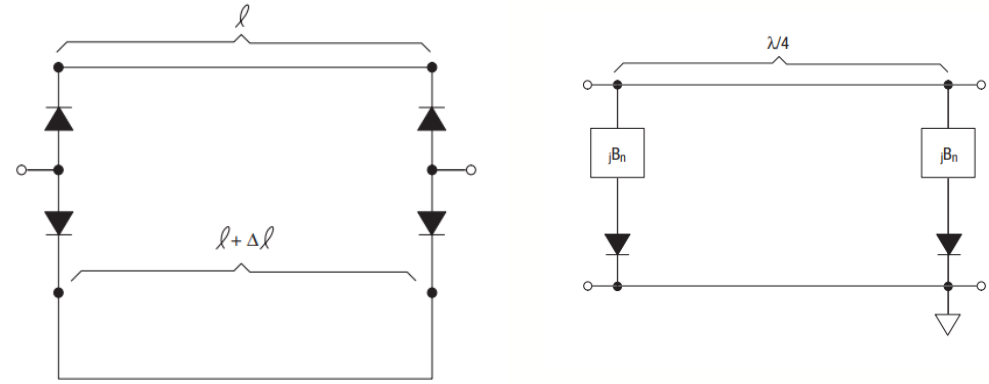
# PIN Diode Phase Shifters

- ▶ A phase shifter is a device that introduces some phase shift into a circuit/ signal
- ▶ Idea is to introduce some switched in reactive element to provide some phase shift
- ▶ Delay lines also work
- ▶ If we have an array of antennas, adding phase shifts can steer the beam




# Phase Shifter Example

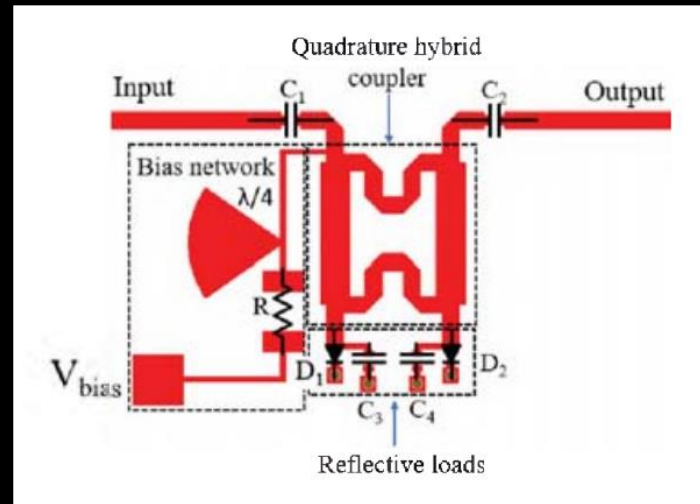

## C. Circuit fabrication



28 mm


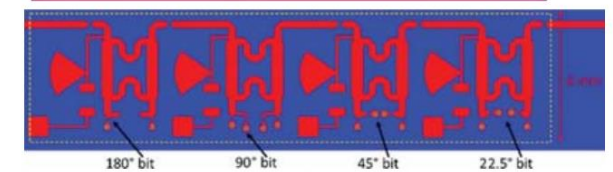


(c)

Ref.	[8]	[9]	[10]	This work*
Technology	CMOS	GaAs	CMOS	PIN diode PCB
Freq. (GHz)	26 - 30	33 - 35	29 - 37	18.7
Bits	5	4	4	4
RL (dB)	NA	>12	>11	>15
IL (dB)	<16.5	<14.2	<12.8	4.7
RMS phase error (°)	<3.3	<5	<8.8	1@18.7 GHz

\* Simulated results

# PIN Diode Detectors

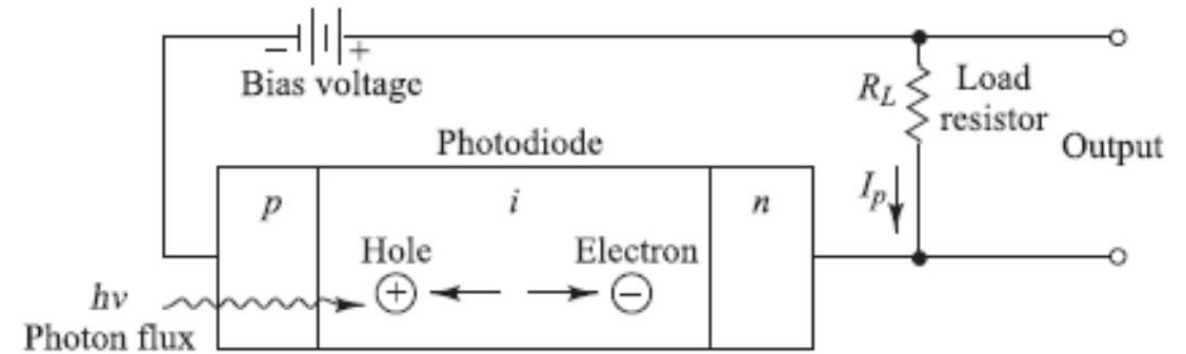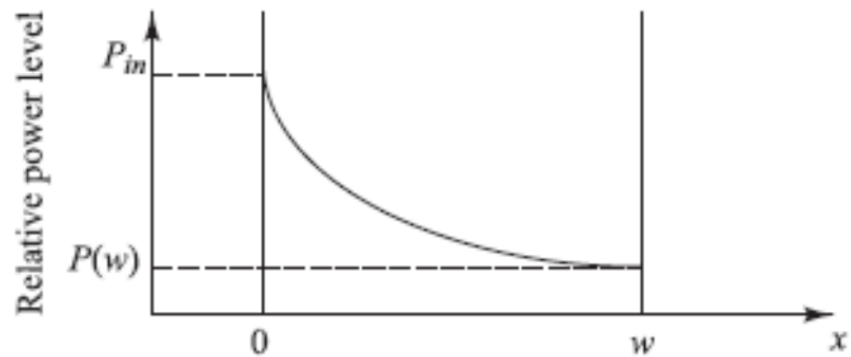

Parameter	Symbol	Unit	Si	Ge	InGaAs
Wavelength range	$\lambda$	nm	400–1100	800–1650	1100–1700
Responsivity	$\mathcal{R}$	A/W	0.4–0.6	0.4–0.5	0.75–0.95
Dark current	$I_D$	nA	1–10	50–500	0.5–2.0
Rise time	$\tau_r$	ns	0.5–1	0.1–0.5	0.05–0.5
Modulation (bandwidth)	$B_m$	GHz	0.3–0.7	0.5–3	1–2
Bias voltage	$V_B$	V	5	5–10	5

# PIN Diode Advantages

- **Ruggedness and High Reliability:** Capable of withstanding high voltage and current peaks and thermal impulses.
- **High Voltage and Current Capabilities:** Suitable for applications requiring voltages greater than 2000 volts and continuous currents exceeding 25 amperes.
- **High Surge Current Capability:** Can handle surge currents over 500 amperes for short durations.
- **Low Distortion:** Exhibits less than -60dBc distortion at 455 KHz.
- **High Power Gain:** Offers a power gain exceeding 10,000:1.
- **Switching Speed:** Capable of switching speeds under 100 ns, depending on construction.
- **Compact Size:** Its small physical size makes it ideal for various applications.
- **Variety of Thermal Packaging Options:** Offers flexibility in thermal management.
- **RF Relay Replacement:** Can replace mechanical (sometimes Hg containing) relays in RF applications.





# PIN Diode Disadvantages

- **Isolation:** Since there is parasitic capacitance in the junction, there will always be some level of leakage when the diode is isolating two different circuits which is usually more than an RF relay, but it really depends on the devices that are being used
- **Repeatability:** The PIN diode is not as repeatable as the RF relay
- **Maximum Power/ Voltage:** The PIN diode does have a maximum power and voltage ratings, which are typically lower than an RF relay
- **Switching Speed:** The reverse recovery time limits the switching speed of the PIN diode. In high speed applications, not all PIN diodes will be acceptable



Questions?

# References

1. W. E. Doherty and R. D. Joos, The Pin Diode Circuit Designers' handbook , [https://www.qsl.net/n9zia/pdf/pin\\_diode\\_handbook.pdf](https://www.qsl.net/n9zia/pdf/pin_diode_handbook.pdf) (accessed Nov. 21, 2023).
2. Skyworks Solutions, Inc., Application note design with PIN diodes , <https://www.digikey.com/Site/Global/Layouts/DownloadPdf.ashx?pdfUrl=AF319B62D6FD4AD182C38082595F3B28> (accessed Nov. 21, 2023).
3. H. Phuong Thao, T. Van Son, N. Van Doai, N. Trong Duc and V. V. Yem, "A novel frequency reconfigurable monopole antenna using PIN diode for WLAN/WIMAX applications," 2015 International Conference on Communications, Management and Telecommunications (ComManTel), DaNang, Vietnam, 2015, pp. 167-171, doi: 10.1109/ComManTel.2015.7394281.
4. P. Song, R. L. Schmid, A. Ç. Ulusoy and J. D. Cressler, "A high-power, low-loss W-band SPDT switch using SiGe PIN diodes," 2014 IEEE Radio Frequency Integrated Circuits Symposium, Tampa, FL, USA, 2014, pp. 195-198, doi: 10.1109/RFIC.2014.6851695.
5. X. Lin, H. -E. Liu, H. -Y. Chang and Y. -C. Wang, "A 25–65 GHz broadband low-LO-driving wide-modulation-bandwidth monolithic BPSK modulator in GaAs PIN diode MMIC process," 2017 IEEE Asia Pacific Microwave Conference (APMC), Kuala Lumpur, Malaysia, 2017, pp. 910-913, doi: 10.1109/APMC.2017.8251597.
6. K. T. Trinh, J. Feng and N. C. Karmakar, "18.7 GHz 4-Bit PIN Diode Reflection Type Phase Shifter for Radiometer Phased Array Antenna," 2021 2nd International Conference on Robotics, Electrical and Signal Processing Techniques (ICREST), DHAKA, Bangladesh, 2021, pp. 504-509, doi: 10.1109/ICREST51555.2021.9331208.
7. System, "Si Pin diode," Home, <https://www.macom.com/products/product-detail/MA4FCP200> (accessed Nov. 20, 2023).